

EE 211 Lecture 5

T. H. Ortmeier

Spring, 2006

This week's labs

- Aliasing and Pulse Measurements
- 555 Timers
- Important Note: Next weeks schedule

Comments on WA#2

- Tables were much improved
- Those who didn't get all three data points— what do you do?
- Discussion point— don't just talk about the error
- Relate back to the predictive equation
- Lead resistance is a stretch in this case

Sampling Theorem

To ensure accuracy of sampled signals,

$$f_s > 2f_{highest}$$

where

f_s is the sampling rate of the digitizer

$f_{highest}$ is the highest frequency component of the sampled signal

$$f_{nyquist} = \frac{1}{2} f_{sampling}$$

Aliasing

If the sampling theorem is violated, aliasing occurs—

An illustrated on the web site

<http://www.dsptutor.freeuk.com/aliasing/AD102.html>


Labview “canned” programs

- Acquire Waveform.vi
 - Investigate aliasing


Pulse waveform qualities

- Amplitude
- Maximum
- Rise time
- Fall time
- Pulse width


The ideal pulse train

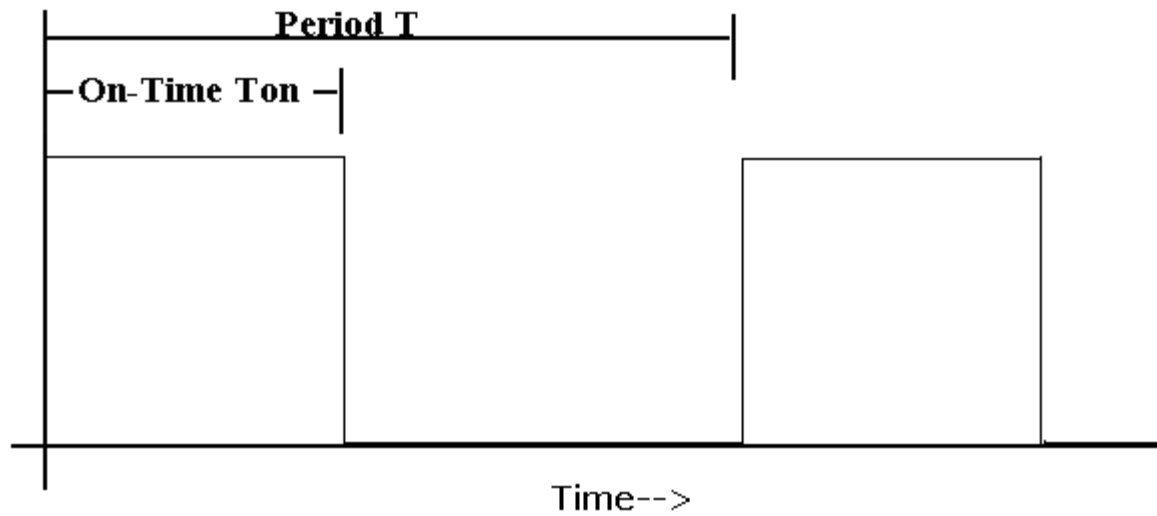

The actual pulse train

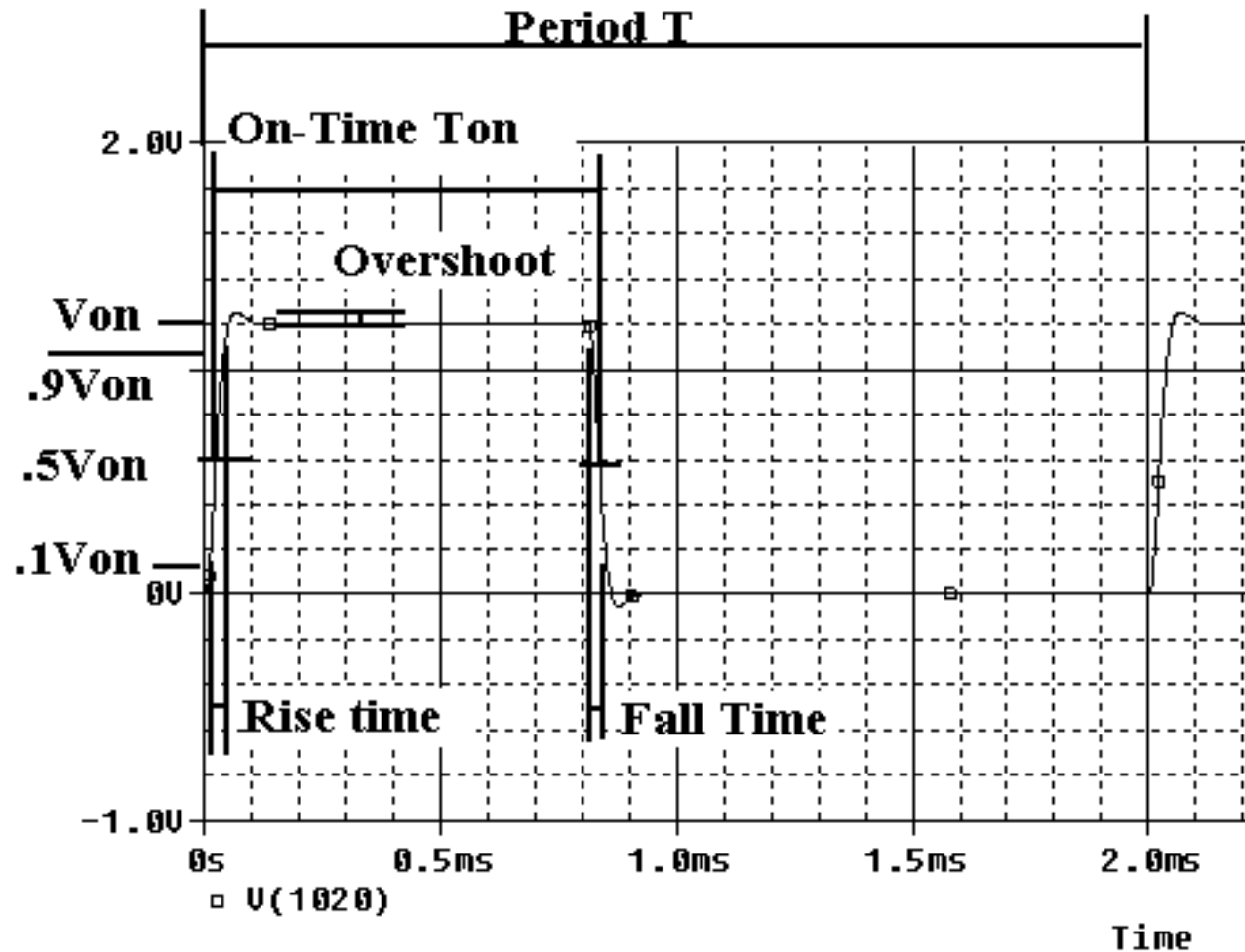

Most circuits

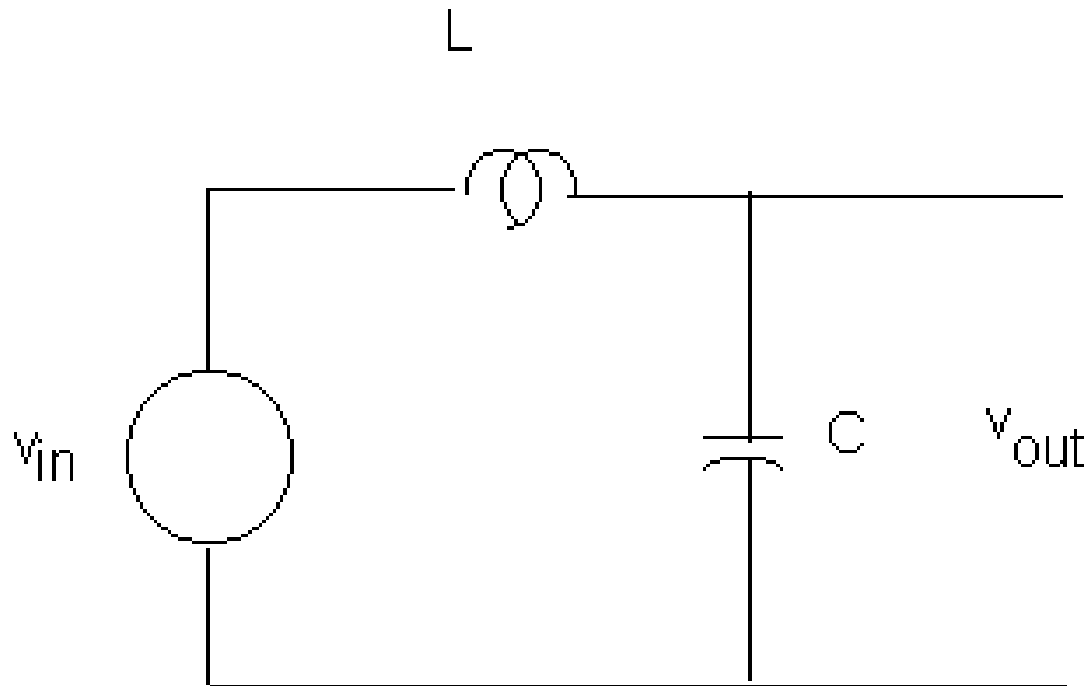

Response to a step input

$$v_o(t) = V_i u(t) \left[1 - e^{-\alpha t} \cos \omega_d t \right]$$

where


$$\omega_d = \sqrt{\omega_o^2 - \alpha^2} = \text{damped frequency}$$

$$\omega_o = \sqrt{\frac{1}{LC}} = \text{natural frequency}$$

$$\alpha = \frac{1}{2RC} = \zeta \omega_n$$

ζ = damping ratio

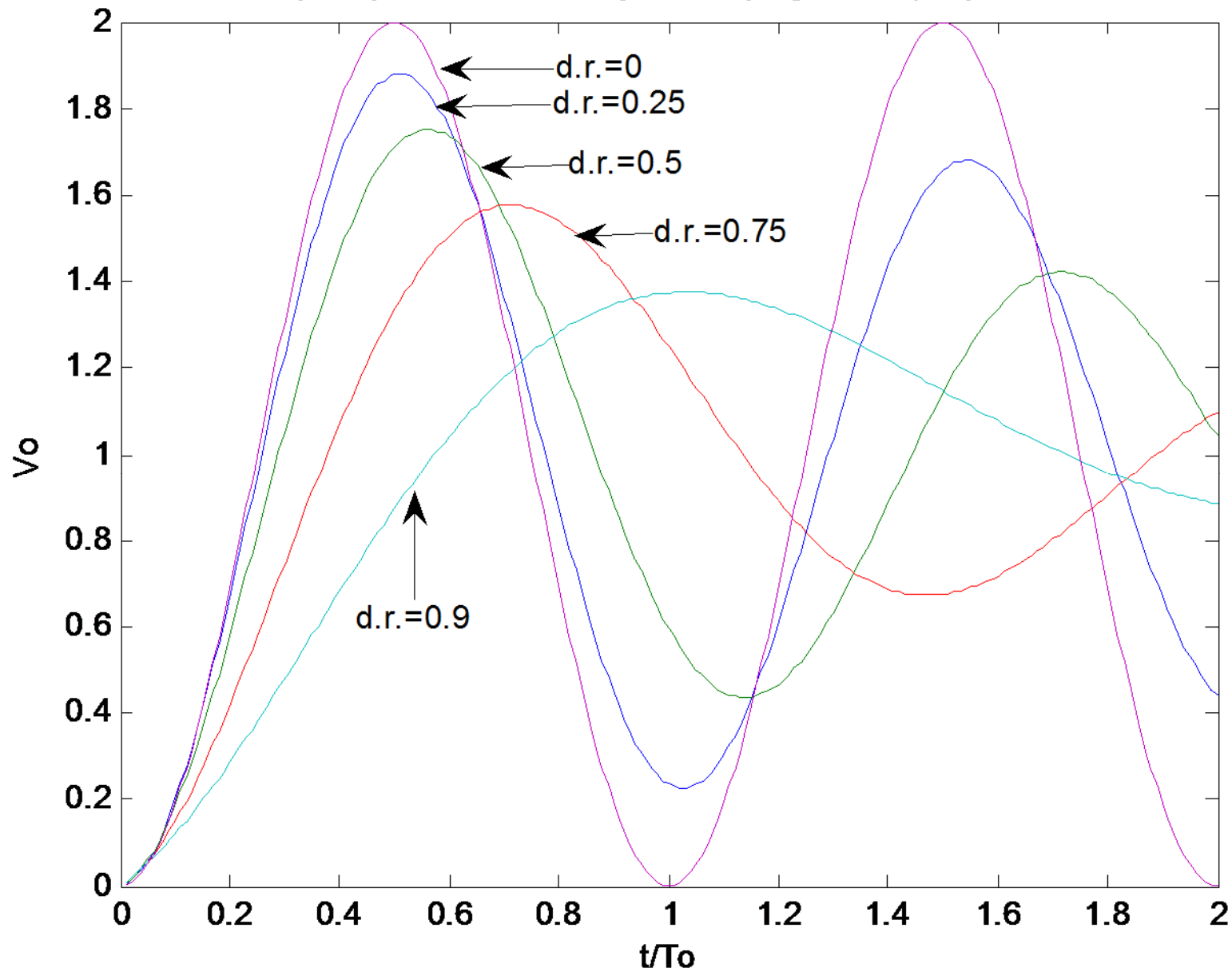Unit step response for a variety of damping ratios (d.r.) less than 1




Goal


- We will measure the effect of varying frequencies on rise times, overshoot, damping, etc.
- Rules of thumb for strays—
 - Inductance ~ 10 nanohenries/inch
 - Capacitance— in the pfd range
- The effect of frequency—hz and mH, khz and uH, Mhz and nH have similar effects

555 Timers

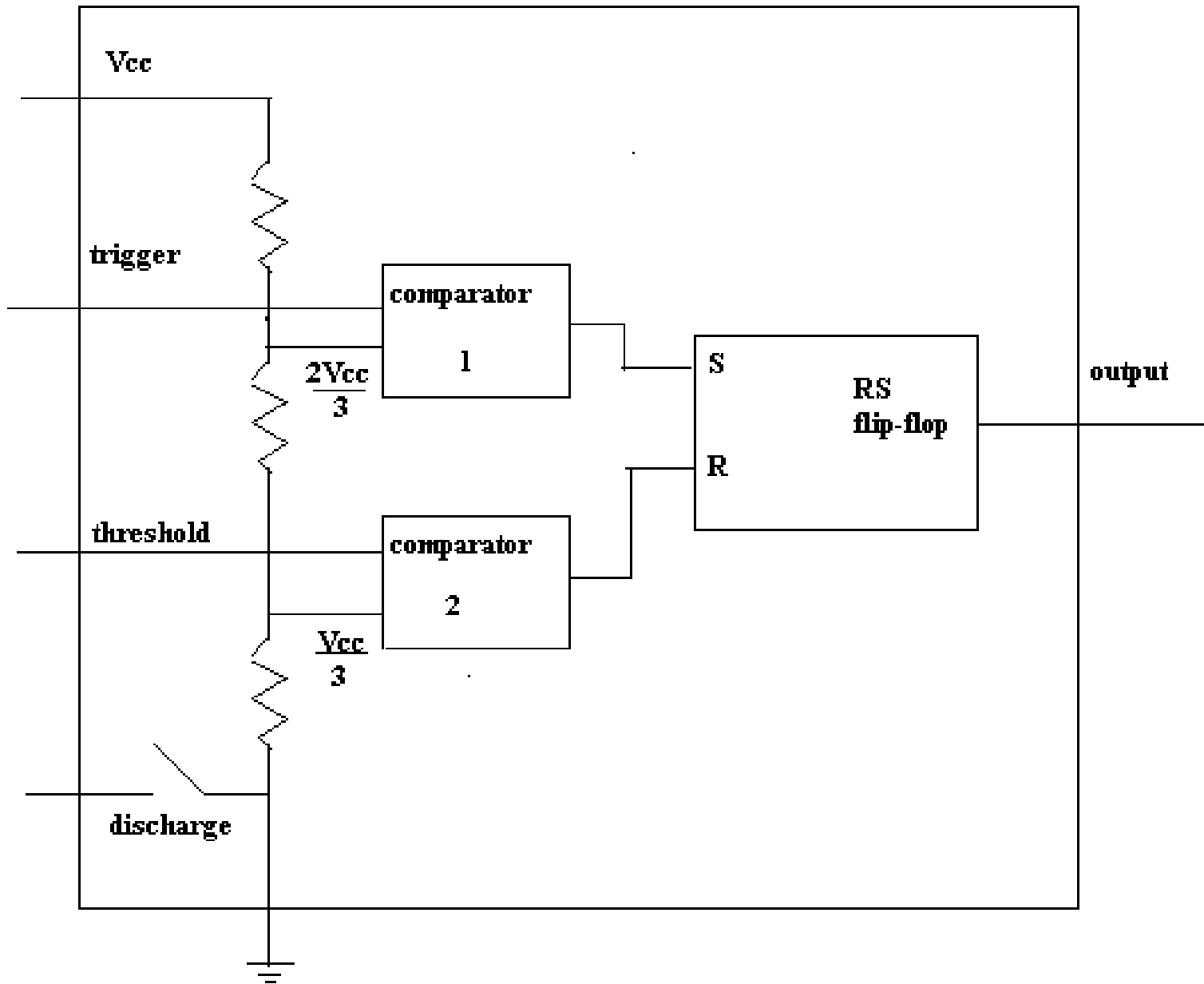
- Precision timing
- Pulse generation
- Sequential timing
- Time delay generation
- Pulse width modulation
- Pulse position modulation
- Linear ramp generator




Astable mode

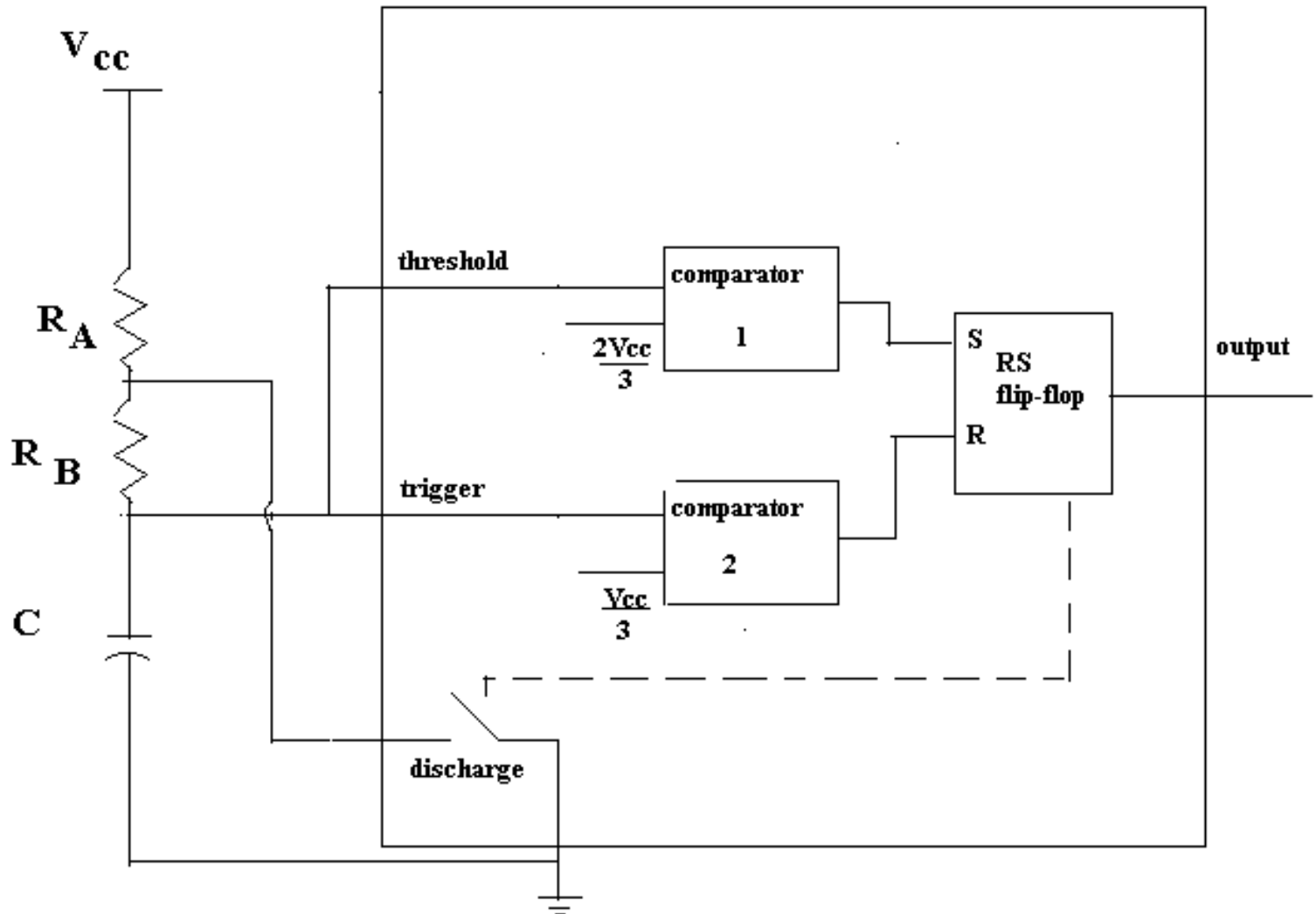


Cap voltage and output voltage

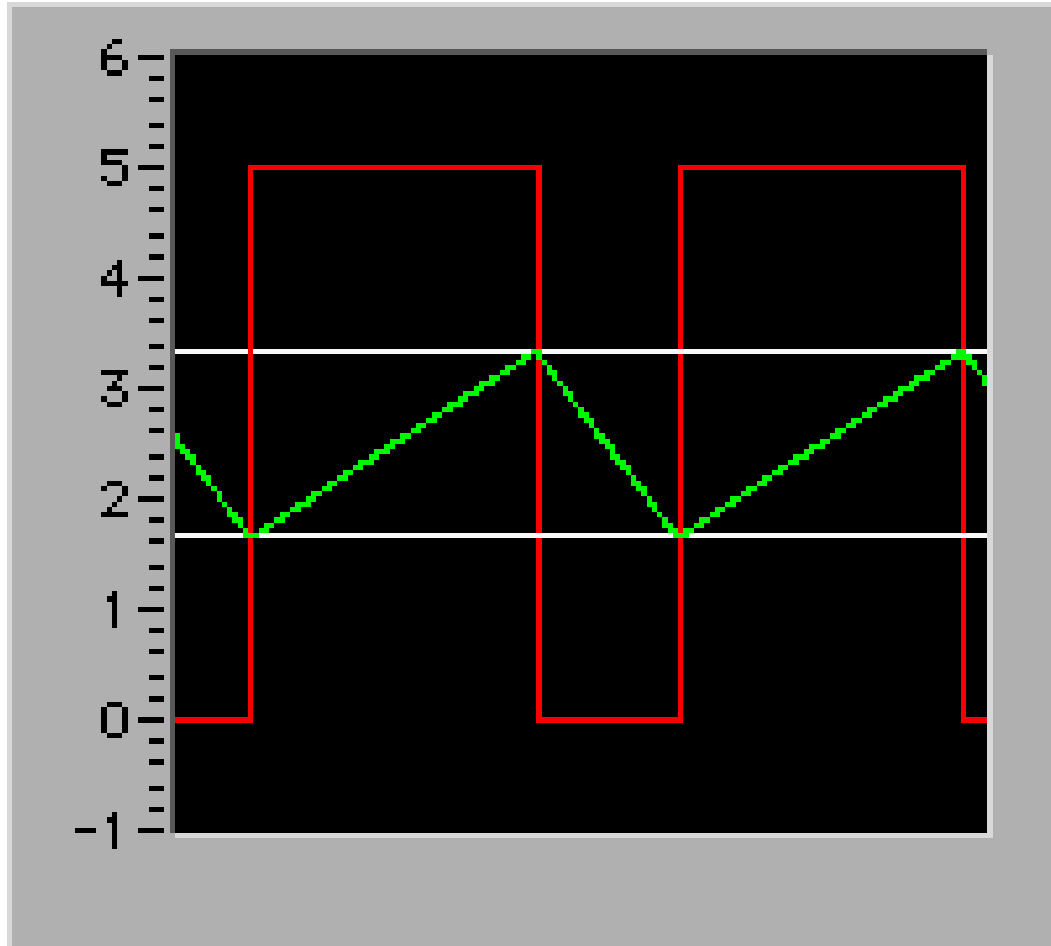

Capacitor charging

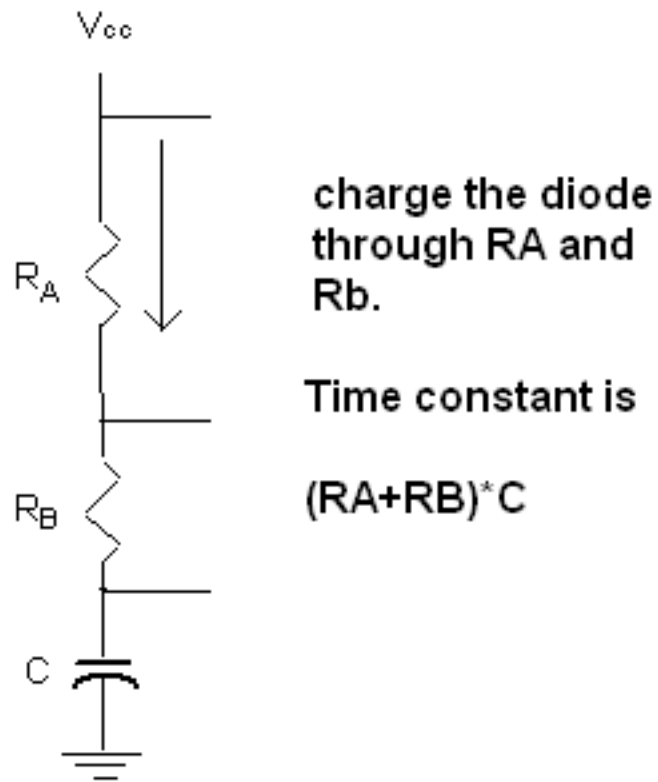

Capacitor Discharge

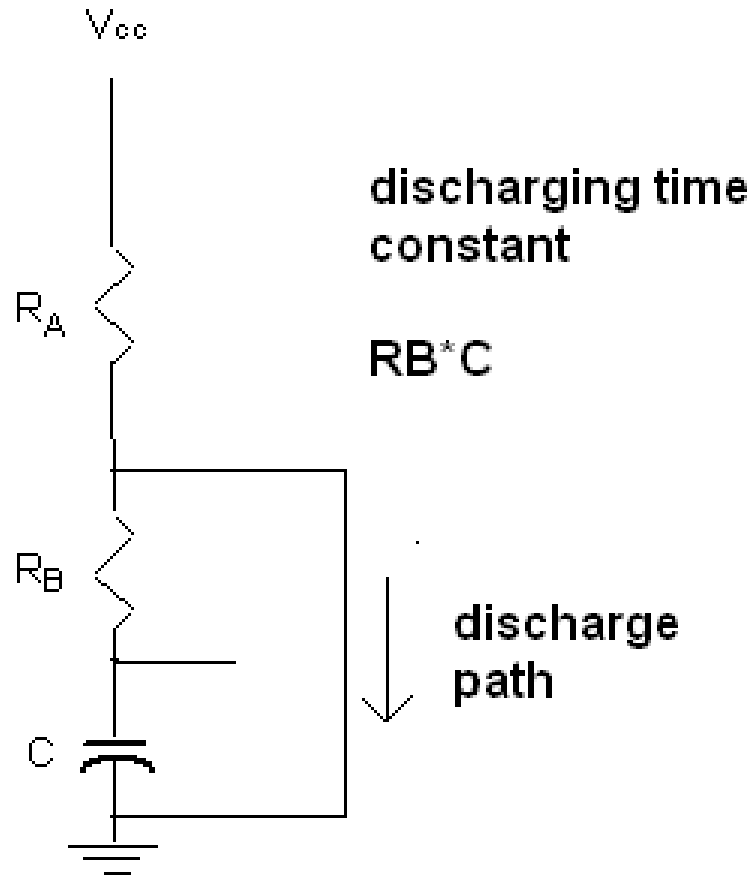

Astable mode

- Charge from $V_{cc}/3$ to $2V_{cc}/3$ —
this takes
$$t_1 = 0.693 (R_A + R_B) * C$$
- Discharging from $2V_{cc}/3$ to $V_{cc}/3$
this takes
$$t_2 = 0.693 R_B * C$$
- The period is $T = t_1 + t_2$

Labs 10 and 11

- We will investigate the astable and monostable modes with Labview modules in Lab 10.
- We will build the astable mode in Lab 11.